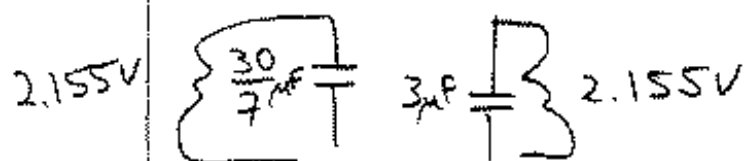


now, we examine the $\frac{30}{7}\mu\text{F}$ combo in parallel with the $3\mu\text{F}$ Combo. The voltage across each is 2.155V .



$$Q = CV$$

$$Q_{3\mu\text{F}} = (3\mu\text{F})(2.155\text{V})$$

$$= 6.465\mu\text{C}$$


$$Q_{\frac{30}{7}\mu\text{F}} = \left(\frac{30}{7}\mu\text{F}\right)(2.155\text{V})$$

$$= 9.236\mu\text{C}$$


$$\text{check } Q_{\text{tot}} = 6.465\mu\text{C} + 9.236\mu\text{C} = 15.7\mu\text{C}$$

great!

so, here's what we have so far

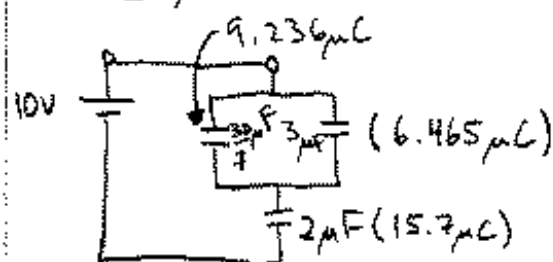

where we want to

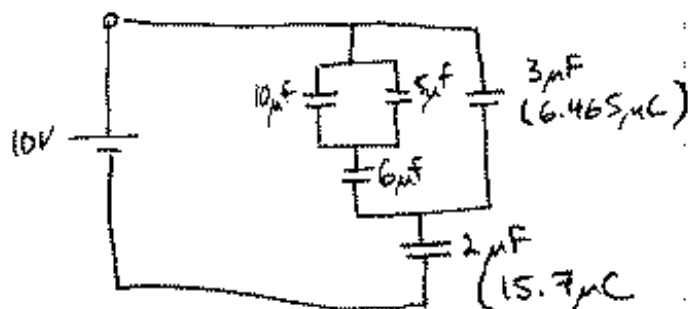

notice that Q on the $\frac{30}{7}\mu\text{F}$ combo is the same as the charge on the $6\mu\text{F}$ cap

Recall

$$\frac{1}{\frac{30}{7}\mu\text{F}} = \frac{1}{15\mu\text{F}} + \frac{1}{6\mu\text{F}} = \frac{1}{10\mu\text{F}} + \frac{1}{5\mu\text{F}} + \frac{1}{6\mu\text{F}}$$

$$\text{so } q \text{ on } 6\mu\text{F} \Rightarrow 9.236\mu\text{C}$$

And we can use the same trick as before


$$2.155V = \text{voltage across } 6\mu F + \text{voltage across } 15\mu F \text{ combo}$$

$$= \frac{9.236\mu C}{6\mu F} + \frac{9.236\mu C}{15\mu F}$$


$$= 1.54V + 0.6157V = 2.156V \text{ close!}$$

so, the voltage across the $15\mu F$ combo is

$$0.6157V$$

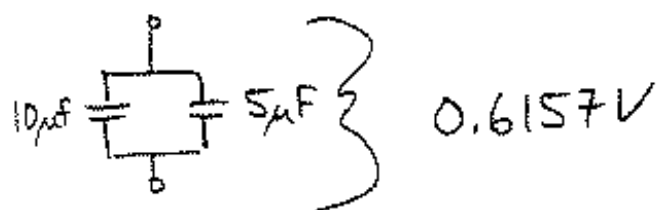

Final

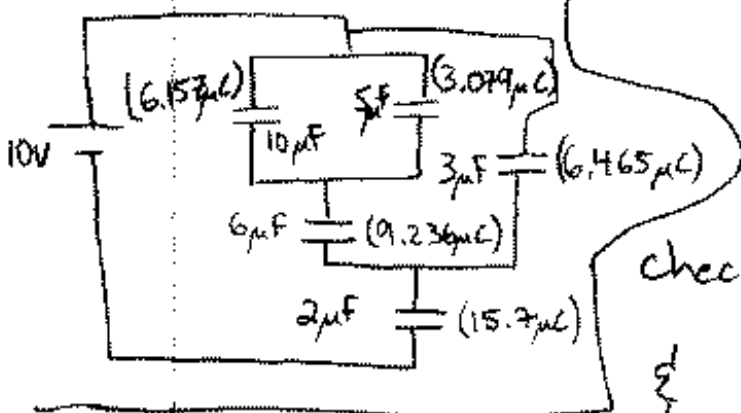

so

$$Q_{5\mu F} = 5\mu F (0.6157V) = 3.079\mu C$$

$$Q_{10\mu F} = 10\mu F (0.6157V) = 6.157\mu C$$

$$\text{check } Q_{5\mu F} + Q_{10\mu F} = 9.236\mu C$$

$$\{ 3.079\mu C + 6.157\mu C = 9.236\mu C \text{ cool!}$$

now, as a check, the potential difference across the $10\mu F + 6\mu F + 3\mu F = 10V$

$$0.6157V + 1.54V + 7.85V = 10.005V \text{ good}$$


We've been talking about resistance.

Recall that

$$R_{ab} = \rho \frac{l}{A}$$



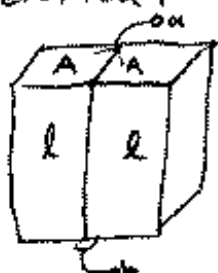Now, like capacitors, we will have to deal with combinations of resistors. Again, consider 2 identical resistors




side by side we get $2 \times \text{Area}$

$$R_{\text{new}} = \frac{\rho}{l_p} (A + A) = \frac{2A}{l_p}$$

$$R_{\text{new parallel}} = \frac{\rho l}{2A}$$

$$\frac{1}{2} R \text{ of } 1$$

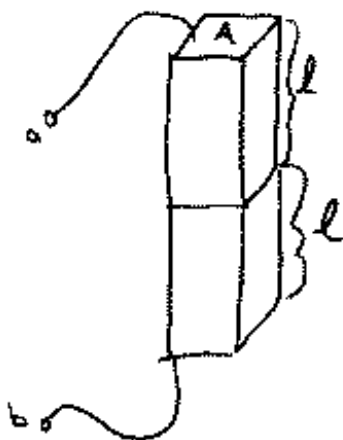

like

$$R_{\text{new series}} = \frac{\rho}{A} (l + l) = 2 R_{\text{one}}$$

Backwards from capacitors!

Resistor

Capacitor

eg n

$$\frac{\rho l}{A}$$

$$\frac{\epsilon_0 A}{d}$$

add areas

parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$C = C_1 + C_2 + C_3$$

add gaps

series

$$R = R_1 + R_2 + R_3$$


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

So how do we motivate this. Very similar to capacitors. We'll use voltage and charge. This time though charge conservation becomes current conservation.

If we have current flow in a conductor


$$I_{in} = I_{out}$$

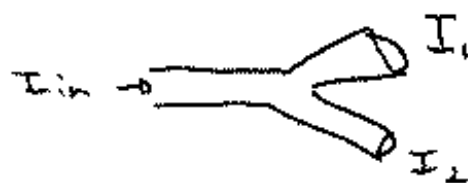& the current is constant
(like we evaluate charge at equilibrium)



$$I_{in} = I_1 + I_2$$

so, in the series combination

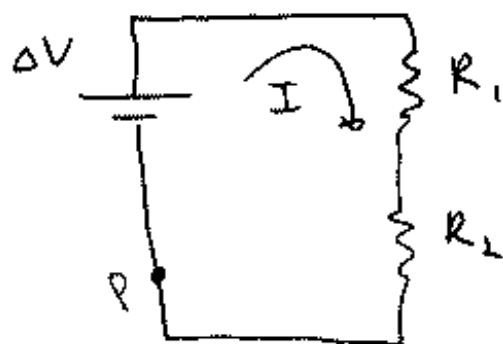

I through R_1 is
the same as I
through R_2

now, if I pick a point on the circuit and follow it in the direction I drew the current, I know: $\{\Delta V \text{ is Potential across } R_1 \& R_2\}$

Charges get a boost in potential as they pass through the battery

Recall, those resistors get hot as current passes through.

So, if we call the point where we started ΔV

get $+\Delta V_{\text{batt}}$ through the battery

lose ΔV_1 as we pass through R_1

ΔV_2 as we pass through R_2

$$0 = \Delta V_{\text{batt}} - \Delta V_1 - \Delta V_2$$

$$= \Delta V_{\text{batt}} - IR_1 - IR_2$$


Since same
I passes through
everything

$$IR_1 + IR_2 = \Delta V_{\text{batt}}$$

$$I(R_1 + R_2) = \Delta V_{\text{batt}}$$

Equivalent

Lets do the same with parallel

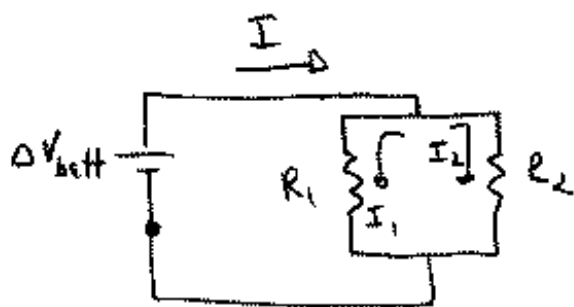

$$\Delta V_{\text{batt}} - I_1 R_1 = 0$$

$$\frac{\Delta V_{\text{batt}}}{R_1} = I_1$$

$$\Delta V_{\text{batt}} - I_2 R_2 = 0$$

$$\frac{\Delta V_{\text{batt}}}{R_2} = I_2$$

$$I_1 R_1 = I_2 R_2$$


$$I = I_1 + I_2$$

$$= \frac{\Delta V_{\text{batt}}}{R_1} + \frac{\Delta V_{\text{batt}}}{R_2}$$

$$= \Delta V_{\text{batt}} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \Delta V_{\text{batt}} \left(\frac{1}{R_{\text{equiv}}} \right)$$

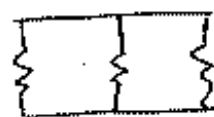So, how do we deal with a complicated bunch of resistors? Look at a small piece & as Is current the same through these? Is voltage across the same



voltage across
is same

or



Current through
is same


you can replace these with equivalent resistances

if you see



for instance,
you need
a higher
technique

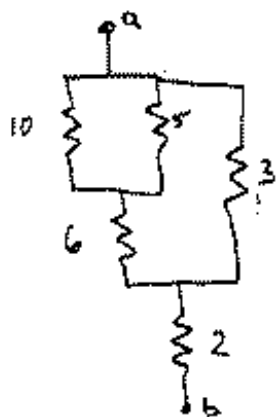lets go through an
example of equivalent resistance that
can be done with our replacements



10 & 5 in parallel


$$\frac{1}{R} = \frac{1}{10} + \frac{1}{5} = \frac{3}{10}$$

$$R = 10/3 \quad (3.33 \Omega)$$



$\frac{10}{3}$ & 6 in series

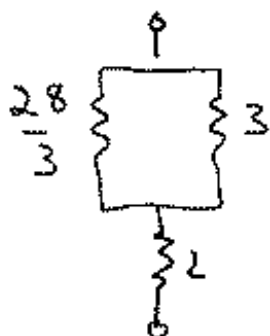
$$R = \frac{10}{3} + 6 = \frac{28}{3} \quad (9.33 \Omega)$$



$\frac{28}{3}$ & 3 in parallel

$$\frac{1}{R} = \frac{1}{3} + \frac{3}{28} = \frac{28}{84} + \frac{9}{84} = \frac{37}{84}$$
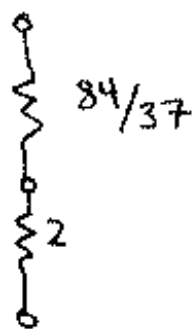
$$R = \frac{84}{37} \quad (2.27 \Omega)$$



$$R_{\text{series}} = 2 + \frac{84}{37} = \frac{74}{37} + \frac{84}{37}$$


$$= \frac{158}{37}$$

$$\sim 4.27 \Omega$$

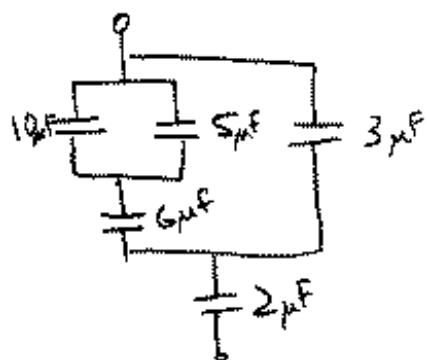(6)


for capacitors you can ask is q same on each
 V across same

lets do the same one
 with caps! (all in μF)



$10 \text{ } \& \text{ } 5$ in Parallel


$$C = 10 + 5 = 15 \mu F$$

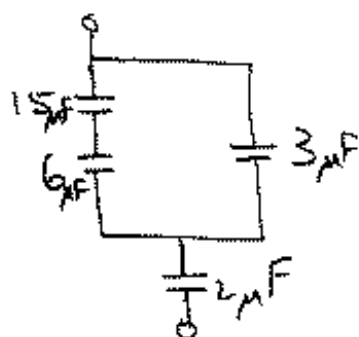


$15 \text{ } \& \text{ } 6$ in series

$$\frac{1}{C} = \frac{1}{15 \mu F} + \frac{1}{6 \mu F} = \frac{2}{30} + \frac{5}{30} = \frac{7}{30}$$

$\frac{30}{7} + 3$ in parallel

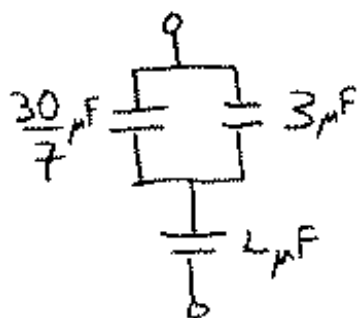
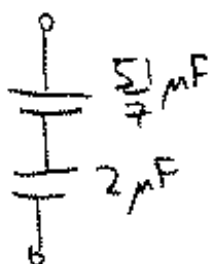
$$C = \frac{30}{7} + 3 = \frac{51}{7} \mu F$$



$\frac{51}{7} \text{ } \& \text{ } 2$ in series

$$\frac{1}{C} = \frac{7}{51 \mu F} + \frac{1}{2 \mu F} = \frac{14}{102} + \frac{51}{102} = \frac{65}{102 \mu F}$$

$$C = \frac{102}{65} \mu F \text{ different}$$

$$= 1.57 \mu F$$

Smallest resistor dominates in parallel

Smallest capacitor dominates in series

Now, let's put a voltage across our combination and try to determine the current in each element

As in your homework, we try to work backwards

Our equivalent resistor looks like



$$I = \frac{\Delta V}{R} = \frac{10V}{4.27\Omega} = 2.34A$$


this means we have 2.34A flowing through



too 2.34A flowing through

2Ω produced a


4.68V potential drop

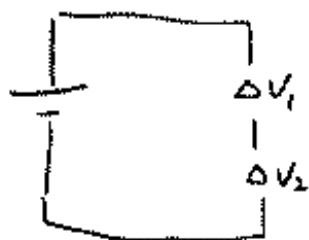

from previous

$$\text{means } \Delta V_1 = 10V - 4.68V = 5.32V$$

so we really simplify the problem

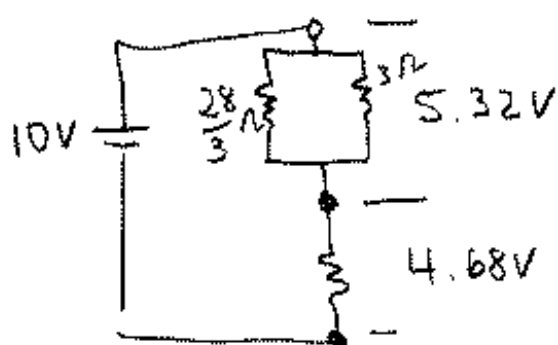


can easily figure out current in each

$$\text{in } 3\Omega, I = \frac{5.32}{3} = 1.77A$$

$$9.333\Omega, I = \frac{5.32}{9.333} = .57A$$

$$I_{tot} = 1.77 + .57 = 2.34A, \text{ cool!}$$

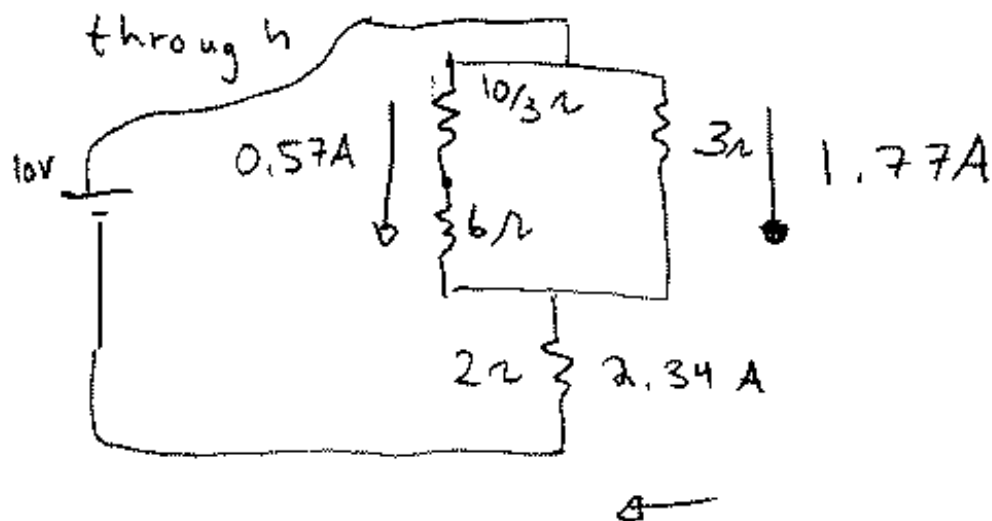
So, we now know that 0.57A flows through h



So the voltage drop across the $\frac{10}{3} \Omega$ is $\frac{10}{3} \cdot .57 = 1.9V$

check Voltage across 6Ω is $6\Omega(.57A) = 3.42V$

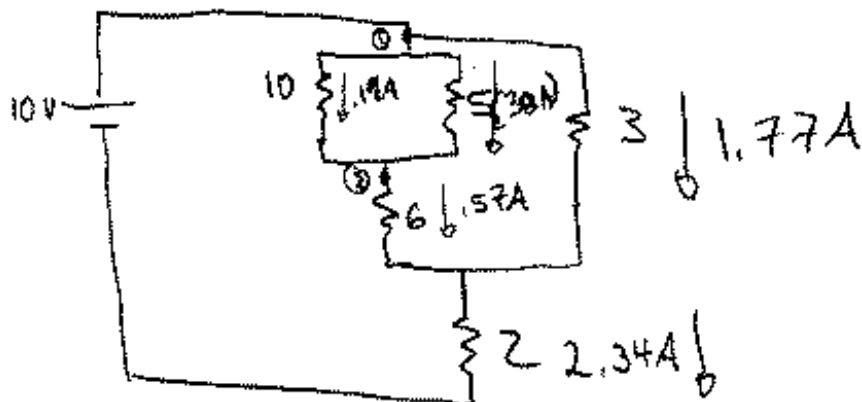ΔV_{tot} across $\frac{10}{3} \Omega \text{ \& } 6\Omega = 5.32V$ good!



ΔV between ① and ② is

1.9V

$$I_{10} = \frac{1.9V}{10\Omega} = .19A$$

$$I_5 = \frac{1.9V}{5\Omega} = .38A$$

hottest resistor

$$I_{tot} = 0.19A + 0.38A + 1.77A = 2.34A \text{ all checks}$$

(9)

How about the capacitor system if we put a voltage on it

- look for series $\leftarrow$ same charge


- look for parallel $\leftarrow$ same voltage

our equivalent circuit



$$Q = CV$$
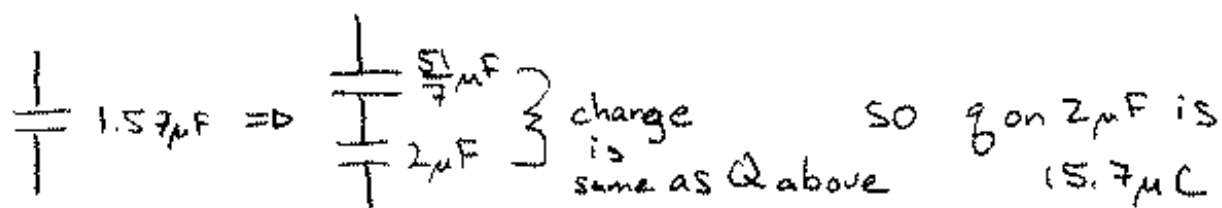
$$= 1.57 \mu\text{F}(10\text{V}) = 15.7 \mu\text{C}$$



We should be able to check this, add up the potential differences on each, we get 10V

$$\overset{\text{should}}{10\text{V}} = \frac{15.7 \mu\text{C}}{(5 \frac{1}{7} \mu\text{F})} + \frac{15.7 \mu\text{C}}{2 \mu\text{F}}$$

$$= 2.155\text{V} + 7.85\text{V} = 10.005\text{V}$$

pretty close

So, we know the potential difference across the $5 \frac{1}{7} \mu\text{F}$ combination is 2.155V.

