

real parallel plate $V = Ed = \frac{\sigma}{\epsilon_0} d = \frac{(q/A)}{\epsilon_0} d$

①

notice $V = q \left(\frac{d}{\epsilon_0 A} \right)$ or $\left(\frac{\epsilon_0 A}{d} \right) V = q$

The amount of charge is determined by the physical layout of the conductors & the applied potential diff

cylindrical $V = 2k\lambda \ln(b/a) = \frac{2}{4\pi\epsilon_0} (q/l) \ln(b/a)$

$\left(\frac{2\pi\epsilon_0}{\ln(b/a)} \right) V = q$

There is a shorthand used to describe this situation that lets us get away with a lot less work, define


$CV = q$

↑ called capacitance


more = more q for same V

Symbol for capacitor is $\frac{||}{|}$ (Some times $\frac{||}{|}$ $\frac{||}{|}$ $\frac{||}{|}$)
like our parallel plate need to look to know

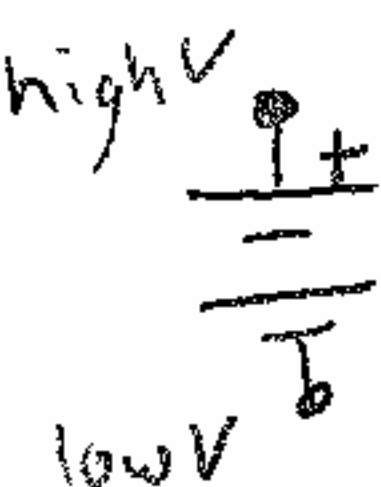Remember, to create that E field we need a source of potential difference, a battery
An ideal battery looks like



when we hook up a capacitor

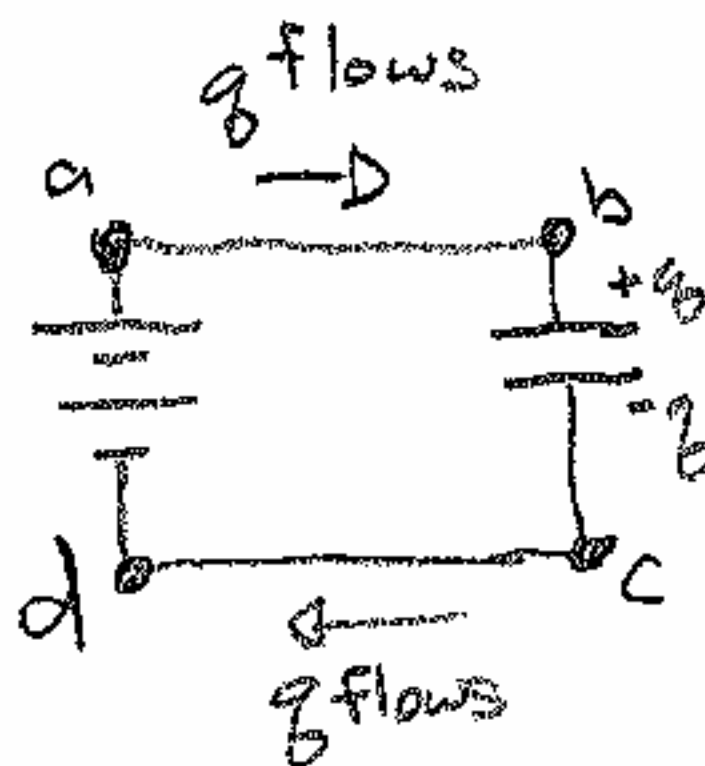

$V_a = V_b$

$V_d = V_c$

$V_a - V_d = V_{batt}$

Unit of Capacitance is called the Farad

(After Micheal Faraday - spent lots of time in basements)
used little math

$$1F = (C/V)$$

Last Friday we had a 30cm long tube with inner radius $15 \times 10^{-6}m$ & outer radius $5.0 \times 10^{-3}m$

$$C = \frac{2\pi (8.85 \times 10^{-12} F/m) 0.30m}{\ln(5 \times 10^{-3} / 15 \times 10^{-6})}$$

$$= 2.9 \times 10^{-12} F = 2.9 pF$$

if we put 2000V across it

$$Q = (2.9 \times 10^{-12} F)(2000V) = 5.8 \times 10^{-9} C$$

Notice for a parallel plate capacitor

$$C = \frac{\epsilon_0 A}{d}$$

to get lots of C
we want a lot of A
very close together (d)

if we want to hold lots of Q, we will want ΔV high

Typically, some sort of ^{insulating} material, or non-conducting oxide is used to get plates close together, & sometimes lot of area is achieved with many layers or by rolling things up.

Consequences

- 1) Electric Field is altered by material
- ϵ_0 replaced by ϵ For C, $\epsilon = \epsilon_0 \epsilon_r$ or $\epsilon = \epsilon_0 / \epsilon_r$ dielect.
dielectric constant
- 2) maximum E may change too before a "lightning strike"

Weakens the field so can put more Q for same ΔV

so

$$Q = CV$$

will have some ϵ max V etc.


Can change things with dielectric material

$$C \Rightarrow \epsilon C_0$$

$\uparrow$ without ϵ

which will have a new value for where the max ΔV we can put on it occurs (called dielectric strength)

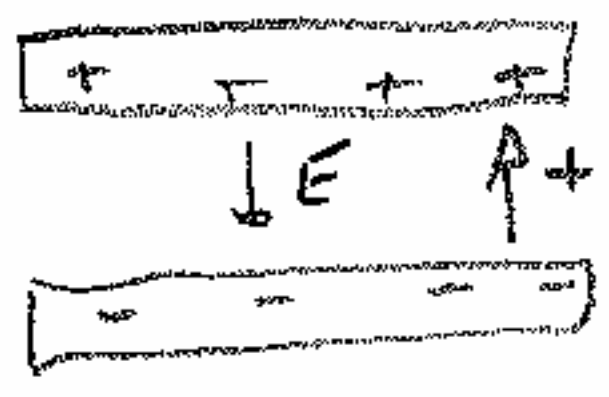It takes energy to "charge up" a capacitor
charging up equivalent to moving one charge between plates




$$\Delta U = (Q_{\text{moved}}) \Delta V_{\text{plates}}$$

$$\text{or } \int dU = \left(\frac{Q_{\text{on plates}}}{C} \right) dQ$$

(little bit moves)

$$= \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} \frac{(CV)^2}{C} = \frac{1}{2} CV^2$$

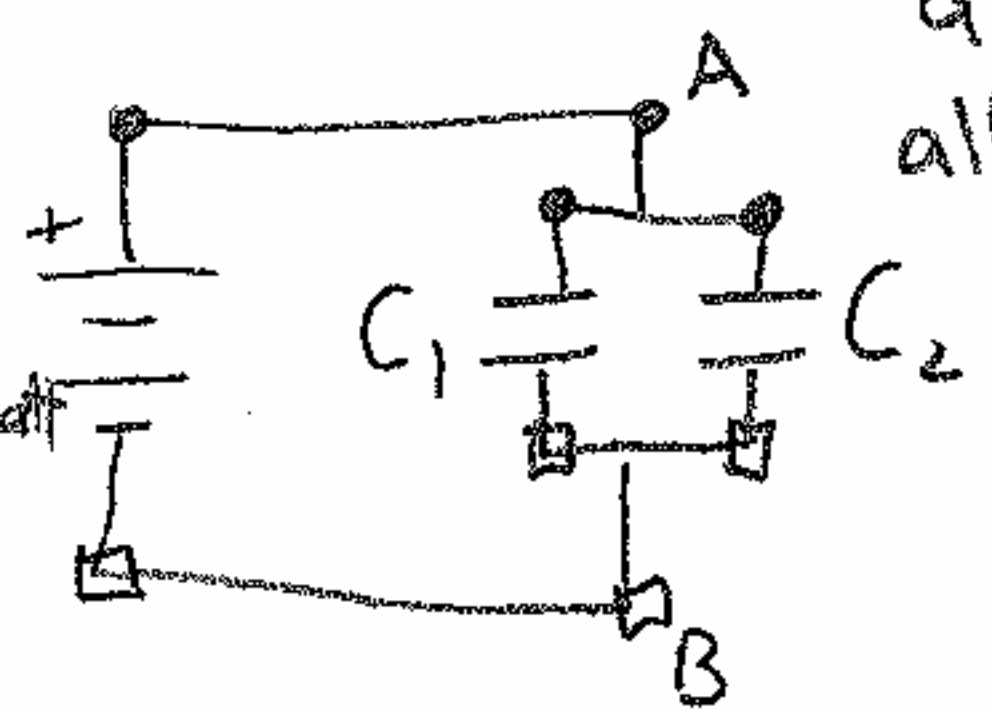Finally, one can use combinations of capacitors to get different values of capacitance. Consider:



all @ same V so V_1 across C_1 is the same as V_2 across C_2 is the same as V_{batt}

$$\left. \begin{aligned} Q_1 &= C_1 V_1 = C_1 V_{\text{batt}} \\ Q_2 &= C_2 V_2 = C_2 V_{\text{batt}} \end{aligned} \right\} \begin{aligned} &\text{total charge that} \\ &\text{flowed from batt} \\ &Q_1 + Q_2 = Q_{\text{batt}} \end{aligned}$$

So, if I wanted to replace the 2 caps w/ one (4)
 between A & B I'd need $C_{one} V_{batt} = q_1 + q_2$


parallel combination (always more)

$$= C_1 V_{batt} + C_2 V_{batt}$$

$$= (C_1 + C_2) V_{batt}$$

$$C_{equiv} = C_1 + C_2 + \dots$$

Consider:

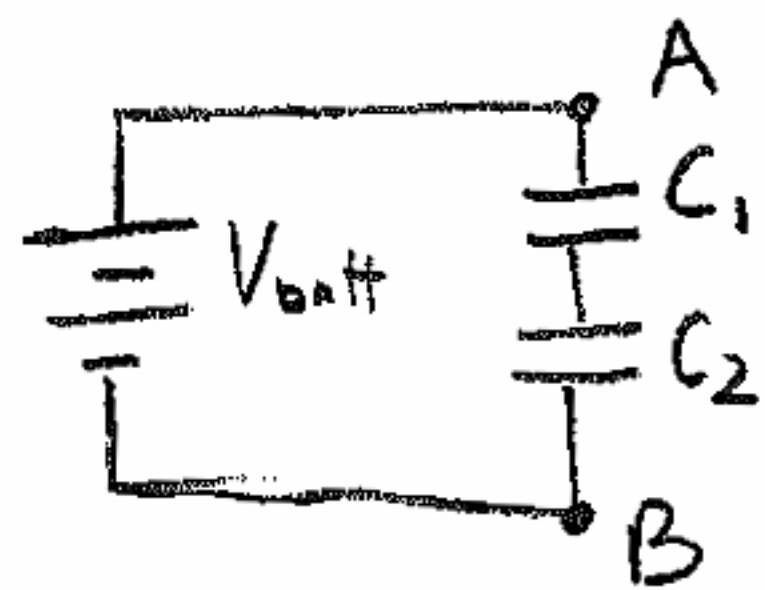


Before we attach the battery, C_1 & C_2 are uncharged (example when not on web)
 This combo can be dangerous!

when q flows from battery onto C_1


So, in this combination,
 $V_1 \neq V_2$ can be different,
 but $q_1 \neq q_2$ are the same
 $Q_{batt} = q_1 = q_2$!

$$V_{batt} = V_1 + V_2 = \frac{q_1}{C_1} + \frac{q_2}{C_2}$$
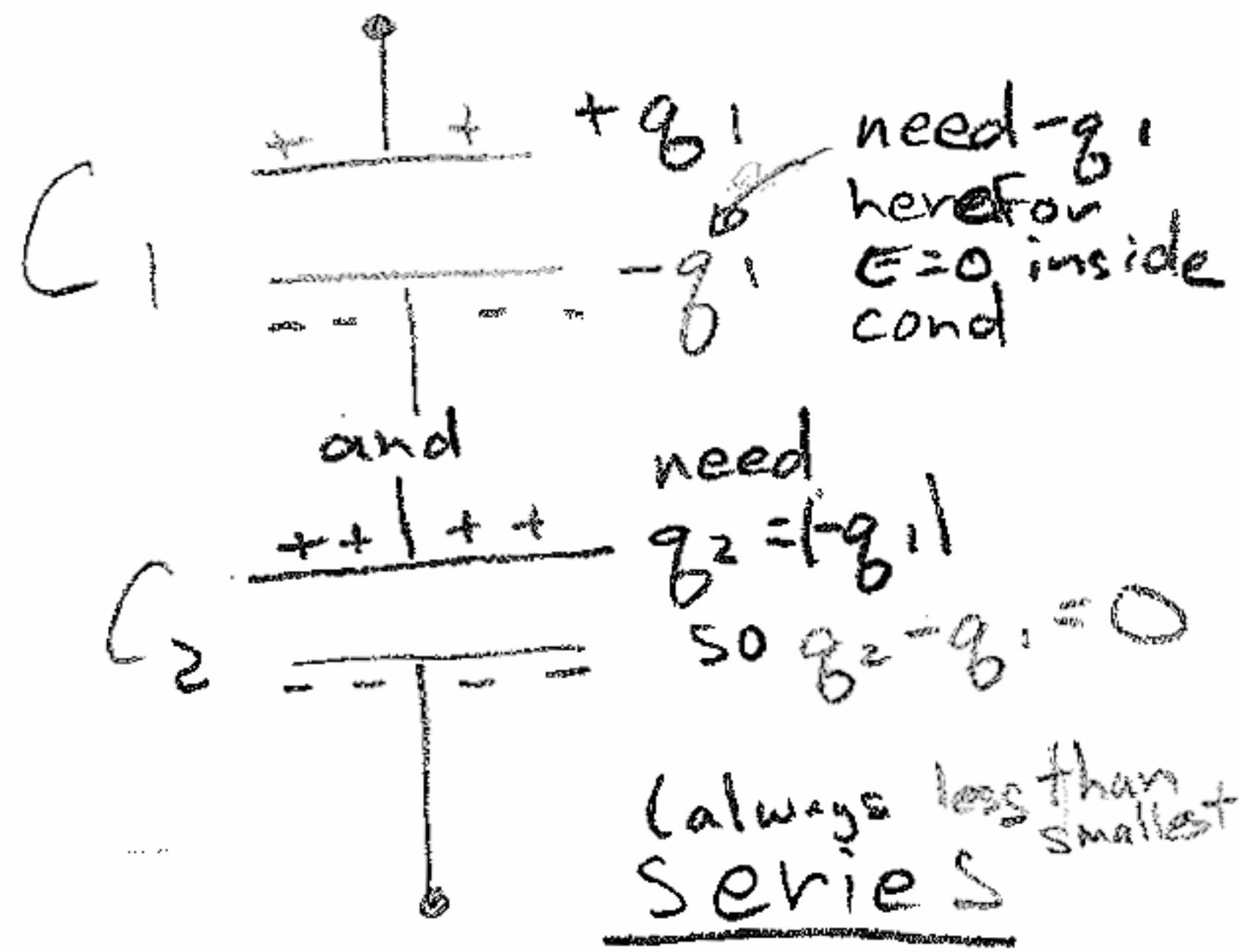
$$= Q_{batt} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = Q_{batt} \left(\frac{1}{C_{equiv}} \right) \quad \text{or} \quad \frac{1}{C_{equiv}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots$$




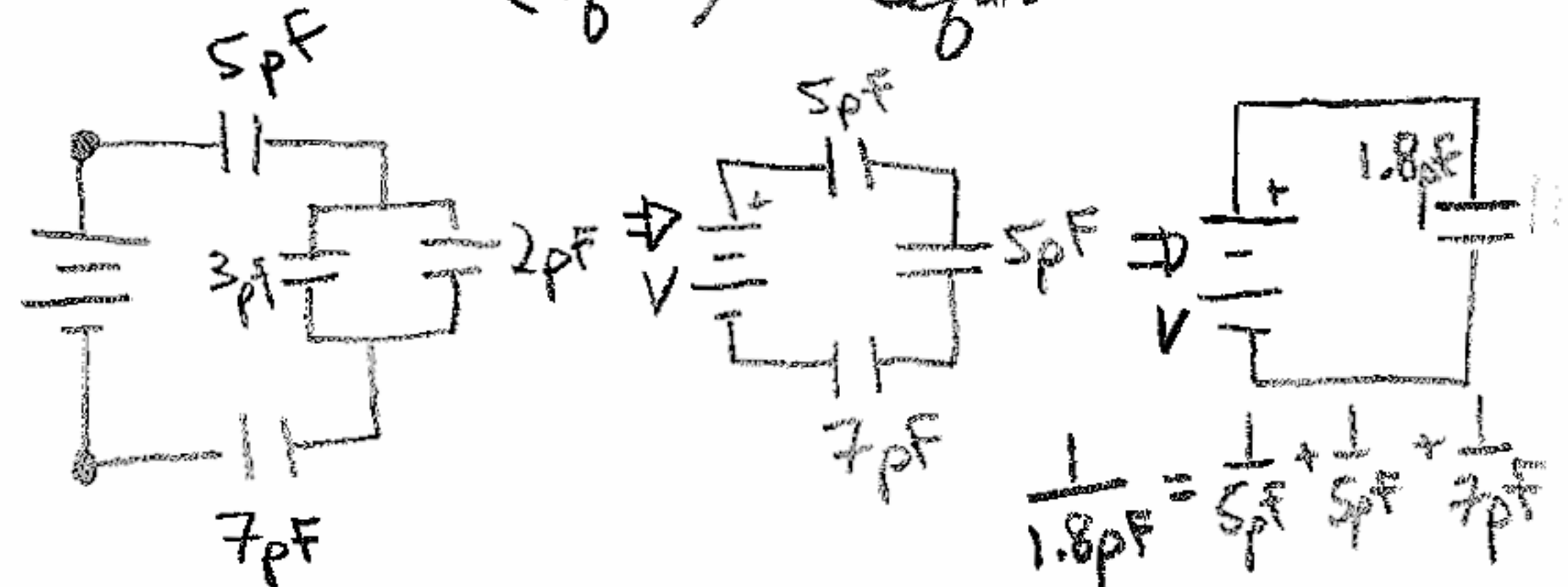More complicated networks are a
 of divide $5V$
 conquer



non-zero q on series caps

①

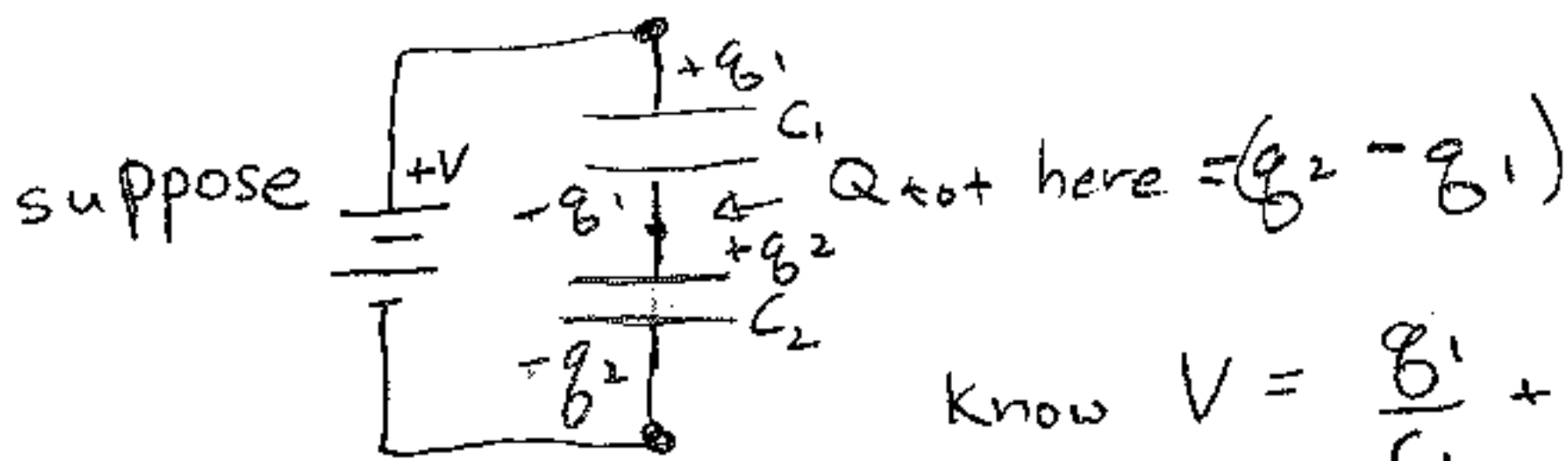

$$\text{know } V = \frac{q_1}{C_1} + \frac{q_2}{C_2}$$

$$Q_{tot} = q_2 - q_1$$

$$Q_{tot} + q_1 = q_2$$

$$V = \frac{q_1}{C_1} + \frac{(Q_{tot} + q_1)}{C_2}$$

$$\left(V - \frac{Q_{tot}}{C_2}\right) = \frac{q_1}{C_1} + \frac{q_1}{C_2} = q_1 \left(\frac{C_2 + C_1}{C_2 C_1}\right)$$

$$\frac{C_2 C_1}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right) = q_1$$


if $Q_{tot} = 0$ (get back C_{eq})

if not $\therefore$ now $V_1 = q_1 / C_1 = \frac{C_2}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right)$

$$\begin{aligned} V_2 = q_2 / C_2 &= \frac{1}{C_2} \left(Q_{tot} + \frac{C_2 C_1}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right) \right) \\ &= \frac{Q_{tot}}{C_2} + \left(\frac{C_1}{C_1 + C_2} V \right) - \frac{C_1}{C_1 + C_2} \left(\frac{Q_{tot}}{C_2} \right) \end{aligned}$$

if $Q_{tot} < 0$, easy to get more ΔV across C_1 than you expect (hence less across C_2)

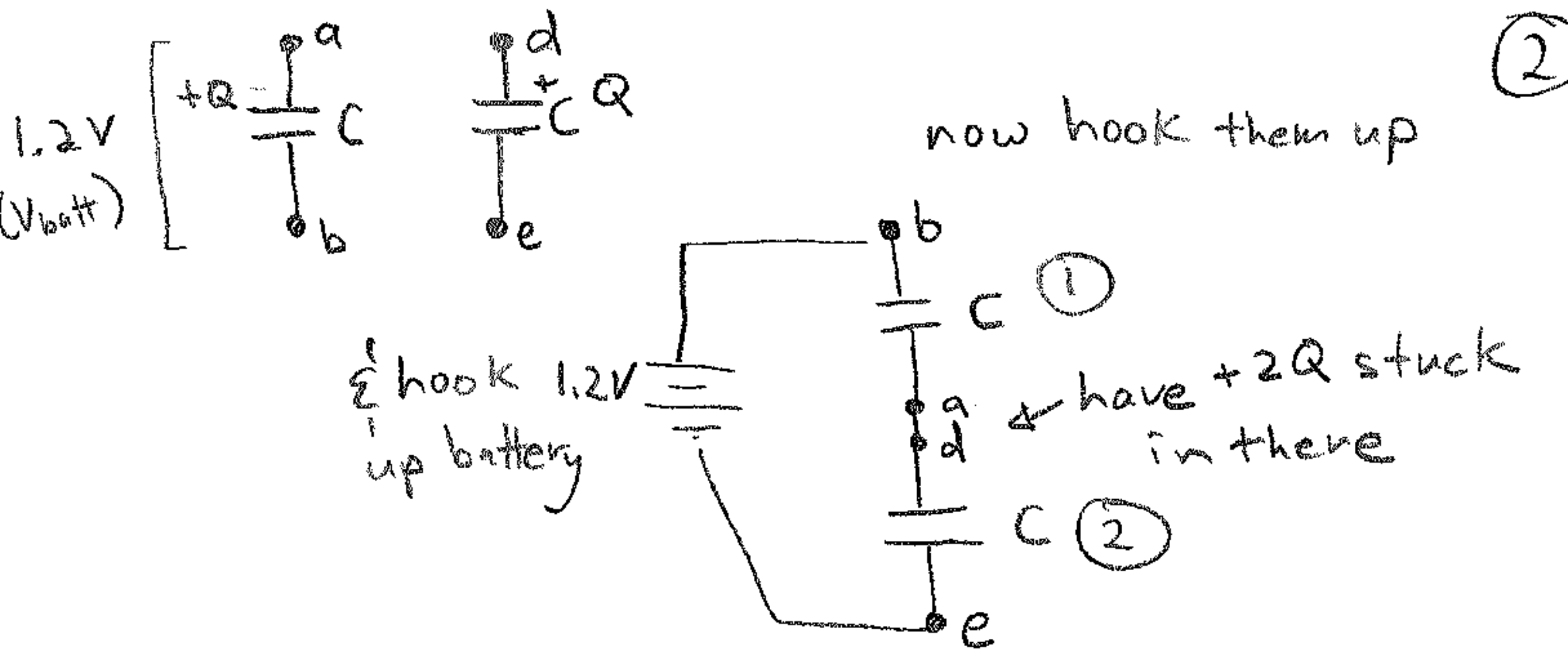Take the example from class. Consider 2 equal capacitors, both charged up to 1.2V;



$$V_1 = \frac{C_2}{C_1 + C_2} \left(V_{batt} - \frac{Q_{tot}}{C_2} \right)$$

$$Q_{tot} = 2Q$$

$$Q = CV_{batt}$$

$$C_1 = C_2 = C$$

$$V_1 = \frac{C}{C+C} \left(V_{batt} - \frac{2CV_{batt}}{C} \right)$$

$$= \frac{1}{2} (V_{batt} - 2V_{batt}) = -V_{batt}/2 \quad (V_2 = \frac{3}{2}V_{batt})$$

If we had connected e to b $Q_{tot} = -2Q$

$$V_1 = \frac{3}{2}V_{batt} \quad (V_2 = -\frac{1}{2}V_{batt})$$

we might have just exceeded the dielectric strength!