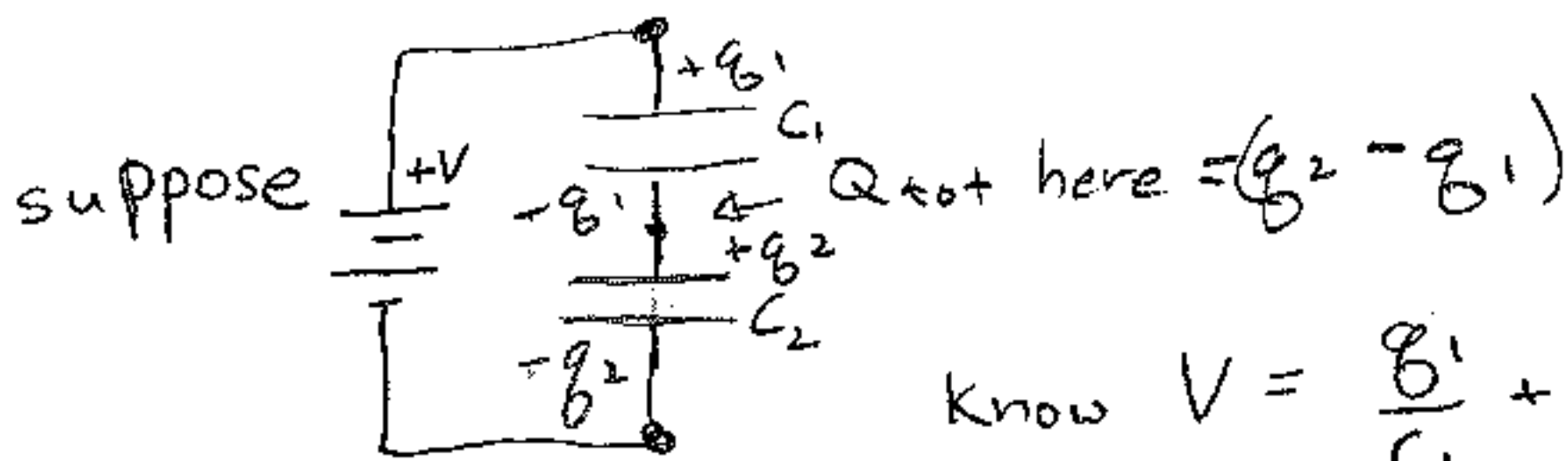


non-zero q on series caps

①



$$\text{know } V = \frac{q_1}{C_1} + \frac{q_2}{C_2}$$

$$Q_{tot} = q_2 - q_1$$

$$Q_{tot} + q_1 = q_2$$

$$V = \frac{q_1}{C_1} + \frac{(Q_{tot} + q_1)}{C_2}$$

$$\left(V - \frac{Q_{tot}}{C_2}\right) = \frac{q_1}{C_1} + \frac{q_1}{C_2} = q_1 \left(\frac{C_2 + C_1}{C_2 C_1}\right)$$

$$\frac{C_2 C_1}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right) = q_1$$


if $Q_{tot} = 0$ (get back C_{eq})

if not $\therefore$ now $V_1 = q_1 / C_1 = \frac{C_2}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right)$

$$\begin{aligned} V_2 = q_2 / C_2 &= \frac{1}{C_2} \left(Q_{tot} + \frac{C_2 C_1}{C_1 + C_2} \left(V - \frac{Q_{tot}}{C_2}\right) \right) \\ &= \frac{Q_{tot}}{C_2} + \left(\frac{C_1}{C_1 + C_2} V \right) - \frac{C_1}{C_1 + C_2} \left(\frac{Q_{tot}}{C_2} \right) \end{aligned}$$

if $Q_{tot} < 0$, easy to get more ΔV across C_1 than you expect (hence less across C_2)

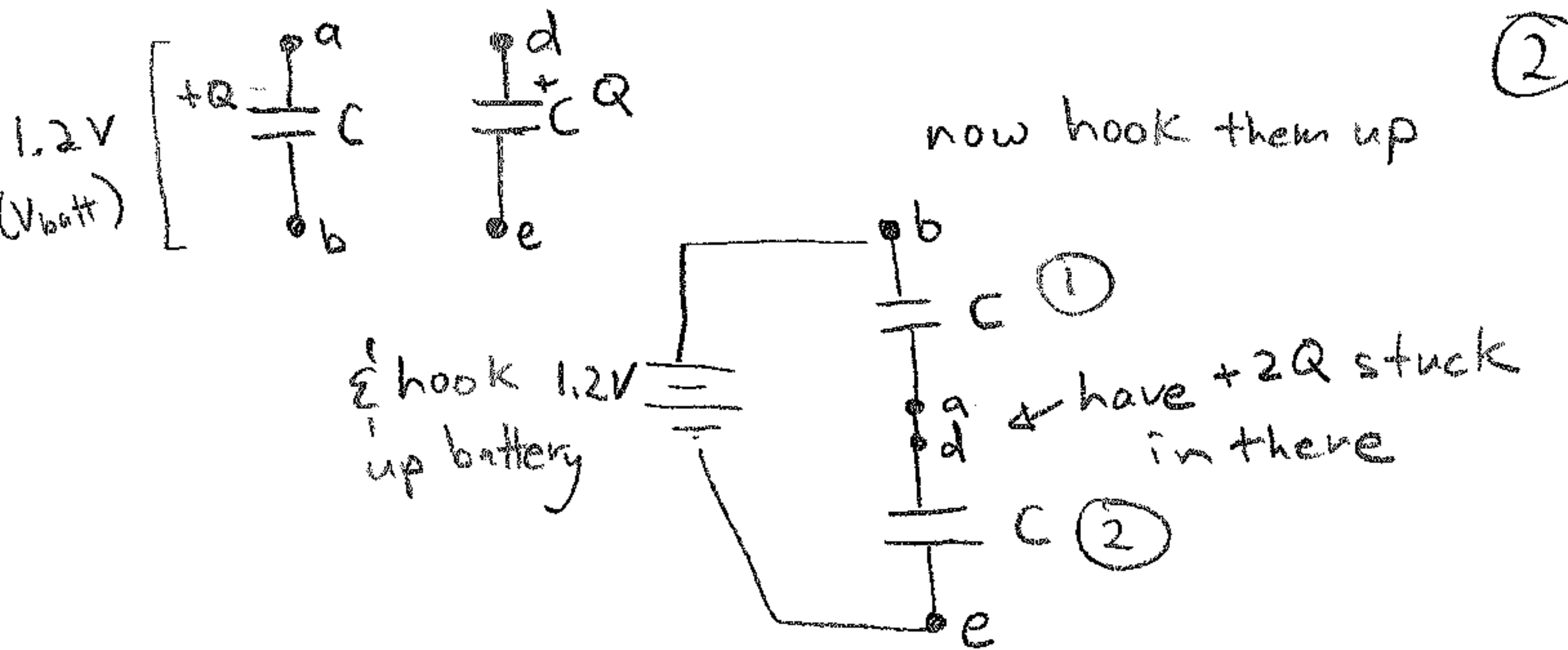Take the example from class. Consider 2 equal capacitors, both charged up to 1.2V;



$$V_1 = \frac{C_2}{C_1 + C_2} \left(V_{batt} - \frac{Q_{tot}}{C_2} \right)$$

$$Q_{tot} = 2Q$$

$$Q = CV_{batt}$$

$$C_1 = C_2 = C$$

$$V_1 = \frac{C}{C+C} \left(V_{batt} - \frac{2CV_{batt}}{C} \right)$$

$$= \frac{1}{2} (V_{batt} - 2V_{batt}) = -V_{batt}/2 \quad \left(V_2 = \frac{3}{2} V_{batt} \right)$$

If we had connected e to b $Q_{tot} = -2Q$

$$V_1 = \frac{3}{2} V_{batt} \quad \left(V_2 = -\frac{1}{2} V_{batt} \right)$$

we might have just exceeded the dielectric strength!