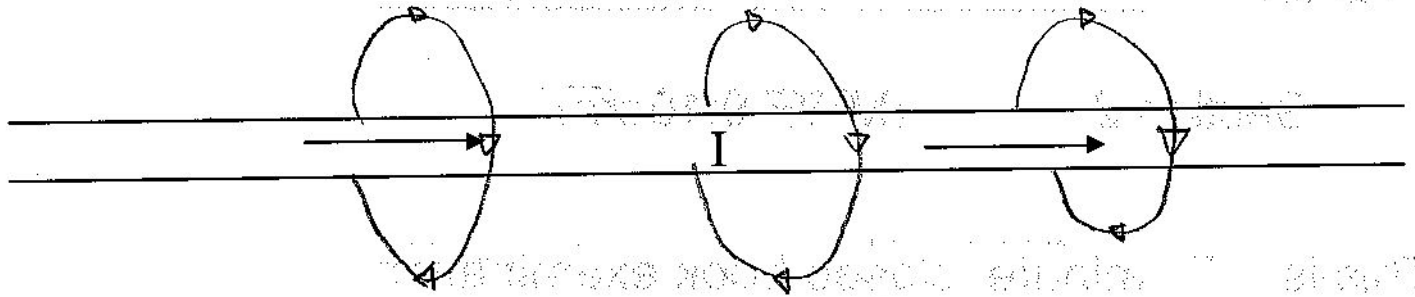


Multiple Choice (2 pts each, show work)

a) Sketch the magnetic field of a wire carrying a current I. (2 pts)



b) A magnetic field of 0.52 T makes an angle with respect to the velocity of a particle with charge 1.0×10^{-12} C traveling at 1000 m/s. If the magnitude of the force on the particle due to the magnetic field is 1.0×10^{-10} N, which of these angles best describes the angle of the magnetic field with respect to the particle velocity? (2 pts)

$$\vec{F} = q\vec{v} \times \vec{B} \quad |\vec{F}| = qvB \sin \theta$$

$$\theta = \sin^{-1} \frac{F}{qvB} = \sin^{-1} \left(\frac{1.0 \times 10^{-10} \text{ N}}{10^{-12} \text{ C} \cdot 1000 \text{ m/s} \cdot 0.52 \text{ T}} \right)$$

- i) 1°
- ii) 5°
- iii) 11°
- iv) 20°
- v) 34°

c) An electron is in a circular orbit in a magnetic field of 1.0 micro-Tesla. What is the magnitude of the angular frequency with which this particle rotates (hint: $\omega = v/r$)? (2 pts)

- i) 60 giga-rads/sec
- ii) 0.11 rads/sec
- iii) 8.8 rads/sec
- iv) 1.0 micro-rads/sec
- v) 18 micro-rads/sec

$$\frac{mv^2}{r} = qvB$$

$$\frac{v}{r} = \omega = \frac{qB}{m} = \frac{1.602 \times 10^{-19} \text{ C}}{9.11 \times 10^{-31} \text{ kg}} \cdot 1 \times 10^{-6} \text{ T}$$

0.18 mega-rads

trouble

d) What is the magnetic field in the center of a 0.25 m long solenoid with 5000 turns that carries 2.0 A? (2pts)

- i) 0.06 Tesla
- ii) 0.05 Tesla
- iii) 130000 Tesla
- iv) 5 micro-Tesla
- v) 1.3 Tesla

$$B = \frac{4\pi \times 10^{-7} \text{ T}}{\text{mA}} \cdot \frac{5000}{0.25 \text{ m}} \cdot 2.0 \text{ A} = B = \mu_0 n I$$

$$= 0.05 \text{ T}$$

Multiple Choice (contd.)

e) With an increase in temperature inside a conductor like tungsten, should you expect the drift velocity to increase, decrease or remain the same?

(Please give a ~ 5 word justification for your answer. You can use formulas in your explanation.)(2pts)

expect ρ to increase, I decreases, V_d decreases
or, less time bet collisions at smaller

(Stay the same.)

(Decrease.)

(Increase.)

f) 2 wires carry identical current and are situated as shown in the figure below. Where must a 3rd wire, which carries an identical current, in an identical direction to the 1st 2 wires, be placed to double the magnetic field at point P due to the original 2 wires? (Draw B directions on figure)(2pts)


i) Point D

ii) Point A

iii) Point B

iv) Point P

v) Point C

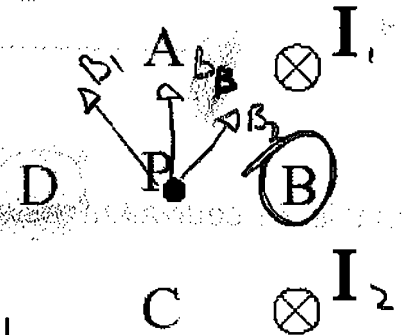

g) An isolated capacitor in air has a stored energy of 1.0 nano-J.

If we now insert a dielectric material of dielectric constant $k=1.3$ into

the gap of the capacitor, what is the new stored energy of the capacitor?

(Hint: Use charge conservation.)(2pts)

i) 1.3 nano-J

ii) 0.77 nano-J

iii) 1.7 nano-J

iv) 0.59 nano-J

v) 1.0 nano-J

$$U_0 = \frac{1}{2} \frac{Q^2}{C} \leftarrow \text{same } Q \Rightarrow U_{\text{new}} = \frac{U_0}{1.3} = 0.77 \text{ nJ}$$

h) What is the resistivity of a conducting wire of length 2.0 m, cross-sectional area of 1.0 mm^2 , and resistance of 1.0 Ohm? (2 pts.)

i) 20 Ohm-m

ii) 2.0 micro-Ohm-m

iii) 1/2 micro-Ohm-m


iv) 20 Mega-Ohm-m

v) 2.0 Ohm-m

$$R = \rho \frac{L}{A} \Rightarrow \rho = \frac{1 \text{ mm}^2 \cdot \left(\frac{1 \text{ m}}{1000 \text{ mm}}\right)^2 \cdot 1.0 \Omega}{2 \text{ m}} = \frac{1}{2} \mu\Omega$$

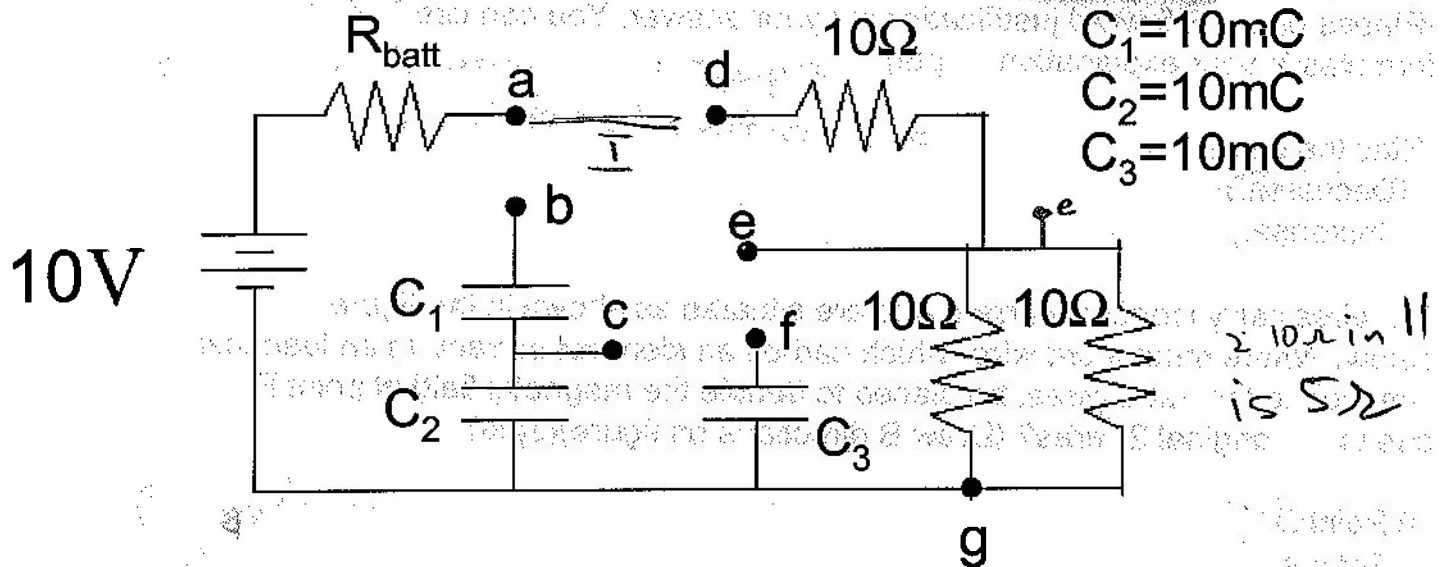2) Circuit (16 pts)

(In the diagram below, all capacitors are initially uncharged. All wires used are conducting wires.)



i) What is the equivalent resistance between points e) and g)?(1pts)

$$\frac{1}{R_{eq}} = \frac{1}{10\Omega} + \frac{1}{10\Omega}$$

$$R_{eq} = 5\Omega$$

$$R_{eq} = 5\Omega$$

ii) What is the equivalent resistance between points d) and g)?(2pts)

$$10\Omega \text{ in series w/ } R_{eq}$$

$$10\Omega + 5\Omega = 15\Omega$$

$$R_{dg} = 15\Omega$$

iii) If point "a" is connected to point "d" with a wire and 0.57 Amps of current flow through R_{batt} , what is R_{batt} ?(3pts)


$$R_{eq \text{ of whole}} = \frac{10V}{0.57A} = 17.54\Omega$$

$$R_{batt} = 2.54\Omega$$

$$17.54\Omega = R_{batt} + R_{dg} = R_{batt} + 15\Omega$$

$$R_{batt} = 2.54\Omega$$

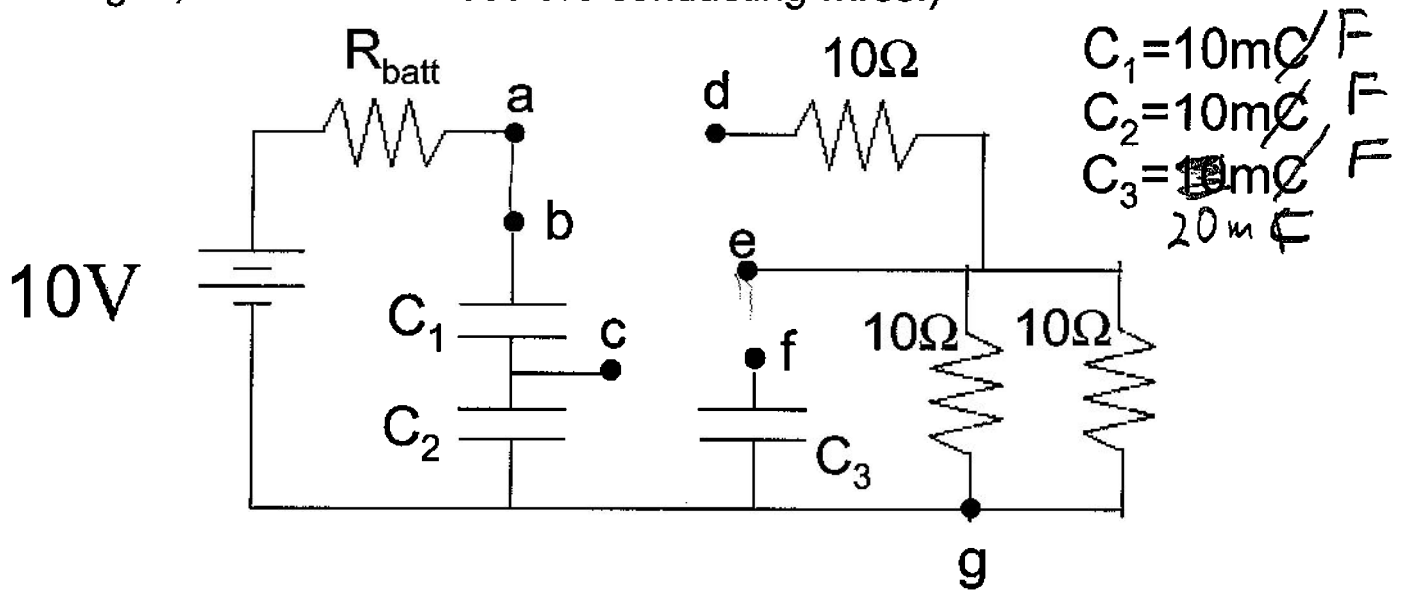2) Circuit (contd.) (In the diagram below, all capacitors are initially uncharged, and all wires used are conducting wires.)



iv) If point "a" is connected to point "b" with a wire, and we wait for the current to stop flowing (i.e. after a very long time), what will be the charge on capacitor C_2 ? (3pts)

Since $C_1 = C_2$, 5V across C_2

$$Q = CV = (10\text{mF})(5\text{V}) = 50\text{mC}$$

$$Q = 50\text{mC}$$

v) Now, the wire between points "a" and "b" is removed without changing the charges (from "after a very long time" in part iv)) on C_1 or C_2 . Then point "c" is connected to point "f" with a wire. What is the charge on C_3 after the charges have stopped moving? (4pts)

connected, V_{same}

$$\frac{Q_2}{C_2} = \frac{Q_3}{C_3} \quad Q_2 + Q_3 = 50\text{mC}$$

$$\frac{3}{2}Q_3 = 50\text{mC}$$

$$Q_2 = \frac{C_2}{C_3} Q_3 = \frac{1}{2} Q_3$$

$$Q = 33.3\text{mC}$$

vi) Now, the wire between points "c" and "f" is removed without changing the charges (from "after the charges have stopped moving" in part v)) on C_1 , C_2 , or C_3 . Then, point "f" is connected to point "e" with a wire. How long will it take the charge on C_3 to go to 10% of its initial value? (3pts)

$$Q(t) = Q_0 e^{-t/RC}$$

$$RC = C_3 R_{\text{eq}} = 20\text{mF} \cdot 5\Omega = 0.1\text{s}$$

$$t = 0.23\text{s}$$

$$0.1/Q_0 = Q_0 e^{-t/0.1\text{s}}$$

$$\ln(0.1) = -t/0.1\text{s}$$

$$t = .23\text{s}$$